

Kirchoff's Laws Exercises:

name: SOLUTIONS

Recall:

In Series Circuits: $I_s = I_1 = I_2 = I_3 = I_4 = \dots$


In Parallel Circuits: $I_s = I_1 + I_2 + I_3 + I_4 + \dots$

In Series Circuits: $V_s = V_1 + V_2 + V_3 + V_4 + \dots$

In Parallel Circuits: $V_s = V_1 = V_2 = V_3 = V_4 = \dots$

SHOW ALL WORK:

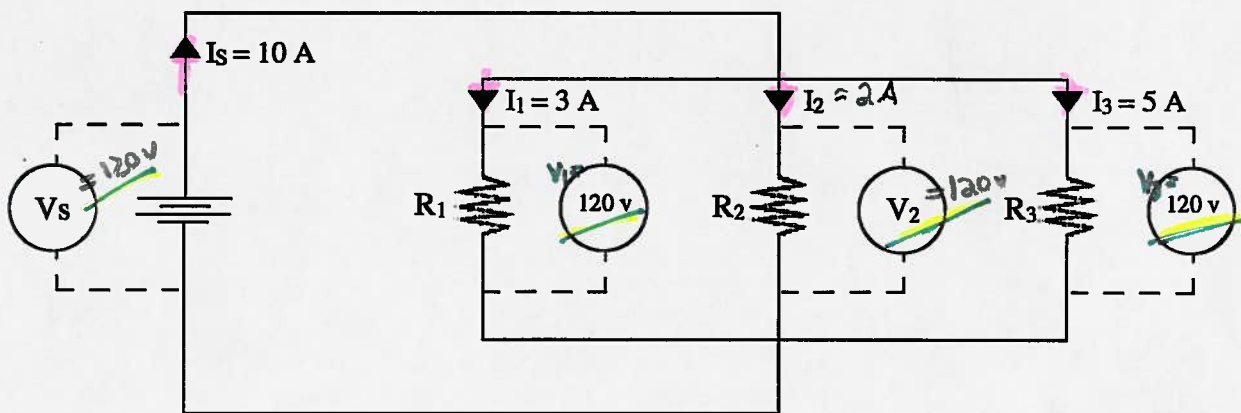1) Study the circuit diagram below and answer the following questions:



a) What is the value of V_2 ? $V_s = V_1 = V_2 = V_3$ (parallel) $V_2 = 120V$

b) What is the value of V_s ? $V_s = V_1 = V_2 = V_3$ (parallel) $V_s = 120V$

c) What is the value of I_2 ? $I_s = I_1 + I_2 + I_3$ (parallel) $I_2 = 2A$
 $10 = 3 + I_2 + 5$

d) What is the Value of R_1 ?

e) What is the Value of R_2 ?

f) What is the Value of R_3 ?

$$R_1 = \frac{V_1}{I_1}$$

$$R_1 = \frac{120}{3}$$

$$R_1 = 40\Omega$$

$$R_2 = \frac{V_2}{I_2}$$

$$R_2 = \frac{120}{2}$$

$$R_2 = 60\Omega$$

$$R_3 = \frac{V_3}{I_3}$$

$$R_3 = \frac{120}{5}$$

$$R_3 = 24\Omega$$

g) Show 2 different ways to calculate the Equivalent Resistance of the entire circuit.

①

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{40} + \frac{1}{60} + \frac{1}{24}$$

$$\frac{1}{R_T} = \frac{9 + 6 + 15}{360}$$

$$\frac{1}{R_T} = \frac{30}{360}$$

$$R_T = 12\Omega$$


②

$$R_T = \frac{V_s}{I_s}$$

$$R_T = \frac{120}{10}$$


$$R_T = 12\Omega$$

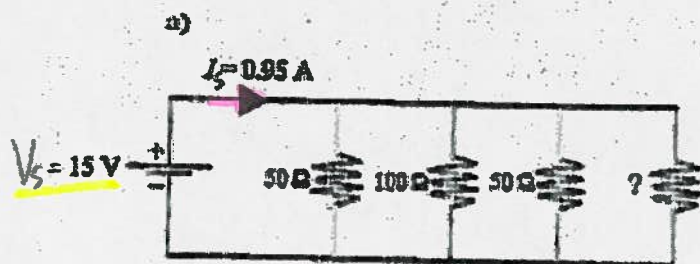2) What is the equivalent resistance of the following circuits?



$$R_T = \frac{V_s}{I_s}$$

$$R_T = \frac{15}{0.95} = 15.8 \Omega$$

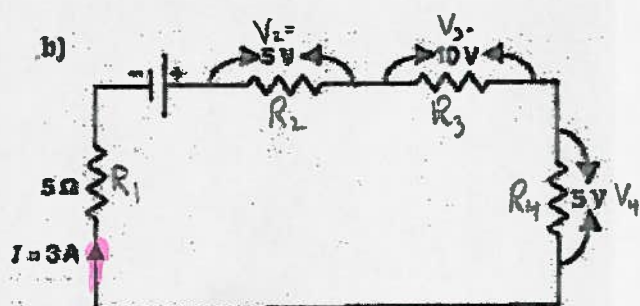


① $I_s = I_1 = I_2 = I_3 = I_4$
(series) $= 3A$

② $R_2 = \frac{V_2}{I_2}$ ③ $R_3 = \frac{V_3}{I_3}$ ④ $R_4 = \frac{V_4}{I_4}$
 $R_2 = \frac{5}{3}$ $R_3 = \frac{10}{3}$ $R_4 = \frac{5}{3}$
 $R_2 = 1.67 \Omega$ $R_3 = 3.33 \Omega$ $R_4 = 1.67 \Omega$

⑤ $R_T = R_1 + R_2 + R_3 + R_4$
(series) $R_T = 5 + 1.67 + 3.33 + 1.67 = 11.67 \Omega$

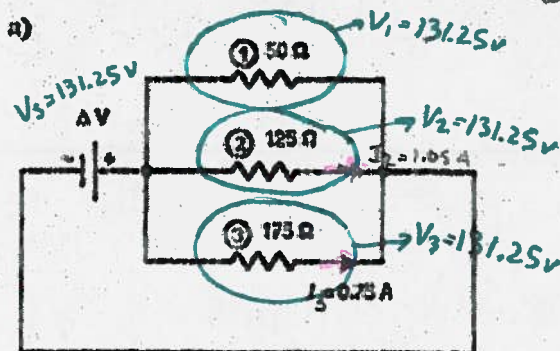
3) What is the current flowing through the no. 2 resistors in the following circuits? $I_2 = ??$




① $V_s = I_s R_3$
 $V_s = 0.75(175)$
 $V_s = 131.25V$

③ $I_2 = \frac{V_2}{R_2}$
 $I_2 = \frac{131.25}{125}$
 $I_2 = 1.05A$

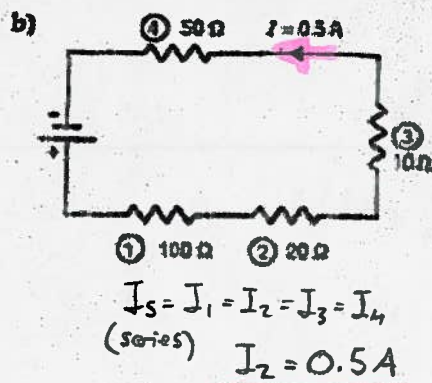② $V_s = V_1 = V_2 = V_3$
(parallel)
 $V_2 = 131.25V$



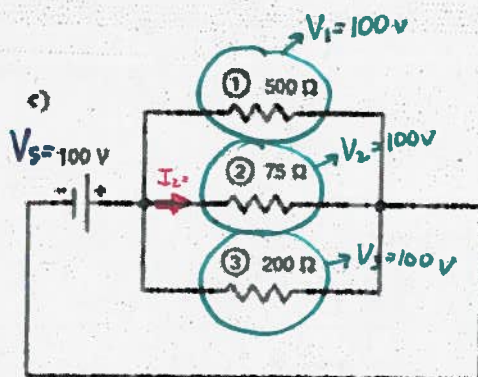
$I_s = I_1 = I_2 = I_3 = I_4$
(series) $I_2 = 0.5A$



① $V_s = V_1 = V_2 = V_3$
 $= 100V$

② $I_2 = \frac{V_2}{R_2}$
 $I_2 = \frac{100}{75} = 1.33A$

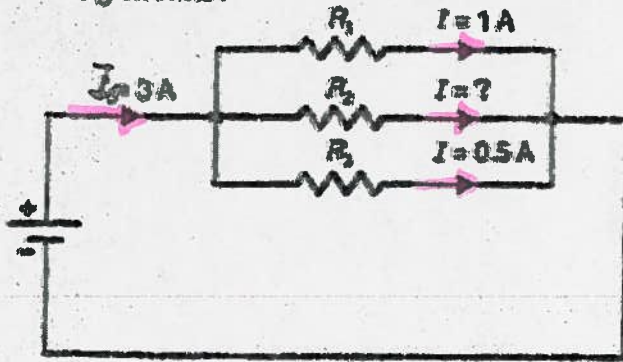- 4) Determine the unknown currents in the following circuits:




$$I_5 = I_1 + I_2 + I_3$$

(Parallel)

$$3 = 1 + I_2 + 0.5$$

$$\underline{I_2 = 1.5A}$$

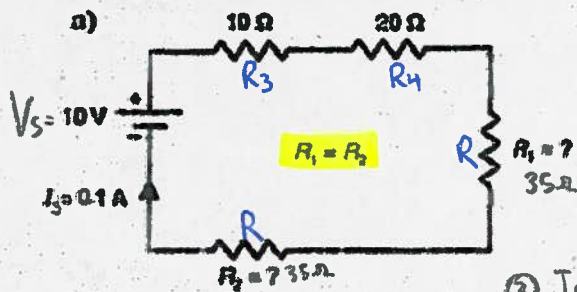- 5) Determine the potential difference across the resistors indicated by a question mark.




$$\begin{aligned} \textcircled{1} R_T &= \frac{V_S}{I_5} \\ R_T &= \frac{10}{0.1} \\ \underline{R_T} &= 100\Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} R_T &= R + R + R_3 + R_4 \\ 100 &= 2R + 10 + 20 \\ 70 &= 2R \\ R &= 35\Omega \\ &\quad (R_1 \text{ \& } R_2) \end{aligned}$$

$$\textcircled{3} I_5 = I_1 = I_2 = I_3 = I_4$$

(Series) $= 0.1A$
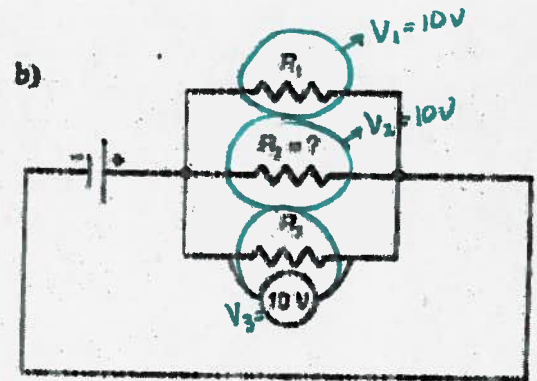
$$\begin{aligned} \textcircled{4} V_1 &= I_1 R_1 \\ V_1 &= 0.1(35) \\ \underline{V_1} &= 3.5V \\ \textcircled{5} V_2 &= I_2 R_2 \\ V_2 &= 0.1(35) \\ \underline{V_2} &= 3.5V \end{aligned}$$




$$V_S = V_1 = V_2 = V_3$$

(Parallel) $= 10V$

- 6) Given the following circuit diagram in which four ammeters have been installed:

Ammeter A_1 reads 7.0 A.
Ammeter A_2 reads 2.0 A.
Ammeter A_3 reads 1.0 A.


What is the reading on ammeter A_4 ?

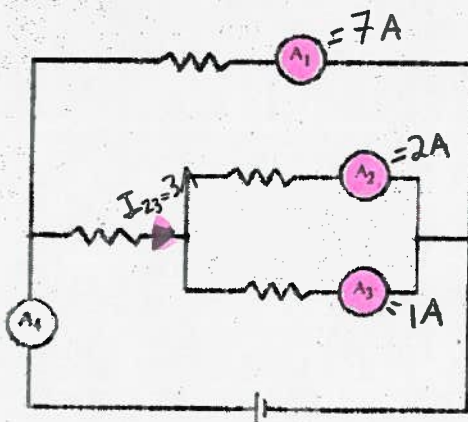

$$\begin{aligned} I_{23} &= I_2 + I_3 \\ \text{(Parallel)} \\ &= 3A \end{aligned}$$

$$\begin{aligned} I_4 &= I_{23} + I_1 \\ I_4 &= 3 + 7 \\ \underline{I_4} &= 10A \end{aligned}$$

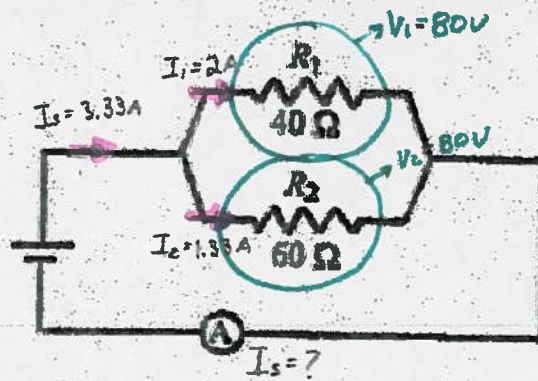- 7) The following circuit consists of a power supply, two resistors (R_1 and R_2) and an ammeter A



$$\begin{aligned} \textcircled{1} V_1 &= I_1 R_1 \\ V_1 &= 2(40) \\ V_1 &= 80\text{V} \end{aligned}$$

$$\begin{aligned} \textcircled{2} V_S &= V_1 = V_2 \\ (\text{Parallel}) &= 80\text{V} \end{aligned}$$

$$\begin{aligned} \textcircled{3} I_2 &= \frac{V_2}{R_2} \\ I_2 &= \frac{80}{60} = 1.33\text{A} \end{aligned}$$

The current through resistor R_1 is 2 A.


What is the current indicated by ammeter A ?

$$\begin{aligned} \textcircled{4} I_S &= I_1 + I_2 \\ (\text{Parallel}) \\ I_S &= 2 + 1.33 \\ I_S &= 3.33\text{A} \end{aligned}$$

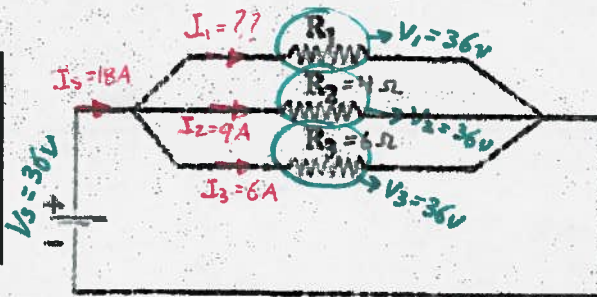- 8) The following circuit is connected to a source that can provide a current intensity of 18 A when the potential difference (voltage) is 36 V?

Place on Diagram

$$\begin{aligned} V_S &= 36\text{ V} \\ I_S &= 18\text{ A} \\ R_2 &= 4\ \Omega \\ R_3 &= 6\ \Omega \\ I_3 &= 6\text{ A} \end{aligned}$$



$$\begin{aligned} \textcircled{1} V_S &= V_1 = V_2 = V_3 \\ (\text{Parallel}) &= 36\text{V} \end{aligned}$$

$$\begin{aligned} \textcircled{2} I_2 &= \frac{V_2}{R_2} \\ I_2 &= \frac{36}{4} \\ I_2 &= 9\text{A} \end{aligned}$$

$$\begin{aligned} \textcircled{3} I_S &= I_1 + I_2 + I_3 \\ 18 &= 6 + 9 + I_3 \\ I_3 &= 3\text{A} \end{aligned}$$

What is the current intensity I_1 flowing through resistor R_1 ?

- 9) Given the following electric circuit with four voltmeters.

Voltmeter V_1 reads 2.0 V.

Voltmeter V_2 reads 4.0 V.


Voltmeter V_S reads 7.0 V.

What is the reading on voltmeter V_3 ?

$$\begin{aligned} V_S &= V_1 + V_2 + V_3 \\ (\text{Series}) \end{aligned}$$

$$7 = 2 + 4 + V_3$$

$$V_3 = 1\text{V}$$

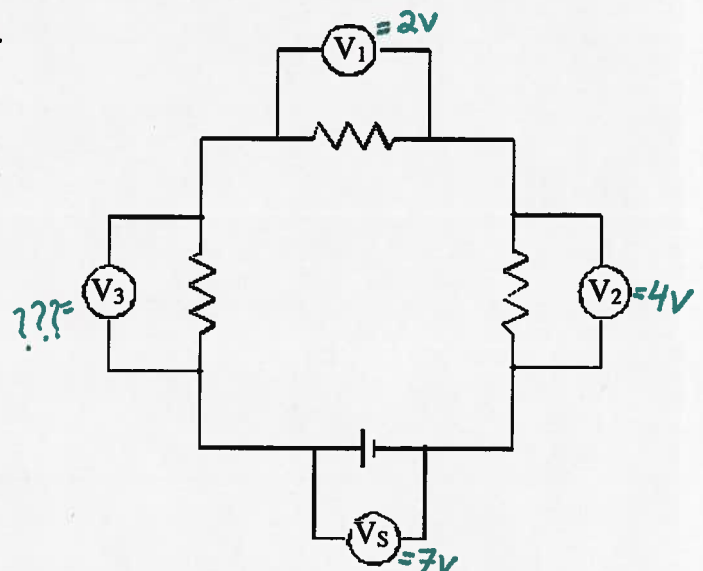

10) The circuit illustrated below consists of a power supply, three resistors (R_1 , R_2 and R_3), an ammeter (A) and a voltmeter (V).

METHOD: 1 What is the potential difference (V) at the terminals of the power supply? (V_s)

$$\textcircled{1} I_s = I_1 = I_2 = I_3$$

(series) $= 2 \text{ A}$

$$\textcircled{2} V_1 = I_1 R_1$$

$$V_1 = 2(10)$$

$$V_1 = 20 \text{ V}$$

$$\textcircled{3} V_2 = I_2 R_2$$

$$V_2 = 2(20)$$


$$V_2 = 40 \text{ V}$$

$$\textcircled{4} V_s = V_1 + V_2 + V_3$$

(series)

$$V_s = 20 + 40 + 60$$

$$V_s = 120 \text{ V}$$

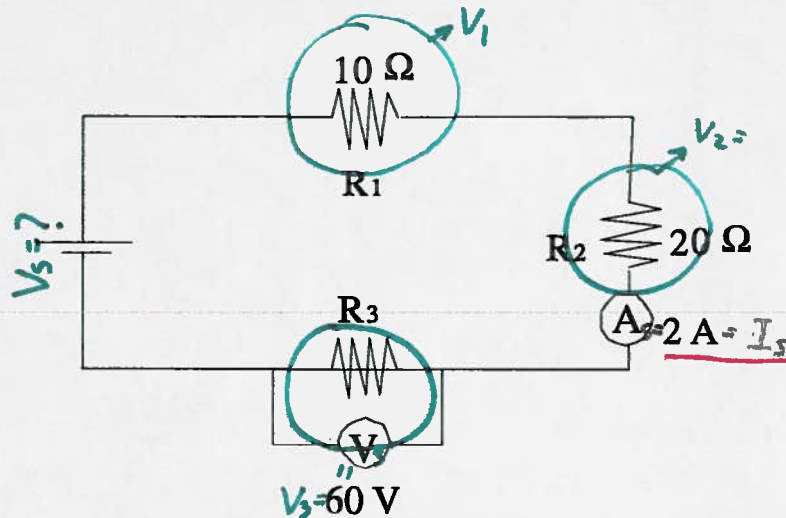

METHOD: 2

$$\textcircled{1} I_s = I_1 = I_2 = I_3$$

(series) $= 2 \text{ A}$

$$\textcircled{2} R_3 = \frac{V_3}{I_3} = \frac{60}{2} = 30 \Omega$$

$$\textcircled{3} R_T = R_1 + R_2 + R_3$$

(series)

$$R_T = 10 + 20 + 30$$

$$R_T = 60 \Omega$$

$$\textcircled{4} V_s = I_s R_T$$


$$V_s = 2(60)$$

$$V_s = 120 \text{ V}$$

11) An electric circuit is illustrated below. The value of the resistors are:

$$R_1 = 50 \Omega$$

$$R_2 = 200 \Omega$$

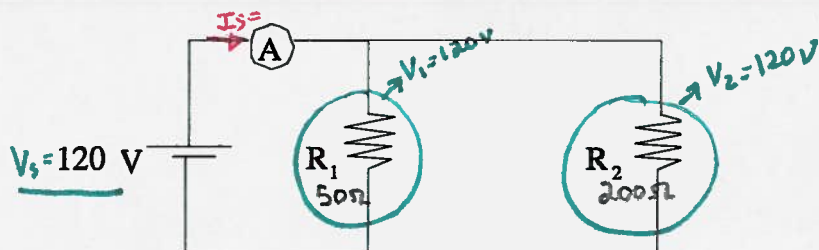

$$\text{a) } \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{50} + \frac{1}{200}$$

$$\frac{1}{R_T} = \frac{4+1}{200}$$

$$\frac{1}{R_T} = \frac{5}{200}$$

$$R_T = 40 \Omega$$

a) What is the value of the equivalent resistance of this circuit?

b) What is the value of the total current read by the ammeter?

$$\text{b) } I_s = \frac{V_s}{R_T}$$

$$I_s = \frac{120}{40} = 3 \text{ A}$$

c) What is the current flowing through R_1 ?

d) What is the current flowing through R_2 ?

$$V_s = V_1 = V_2$$

(parallel) $= 120 \text{ V}$

$$\text{c) } I_1 = \frac{V_1}{R_1}$$

$$I_1 = \frac{120}{50}$$


$$I_1 = 2.4 \text{ A}$$

$$\text{d) } I_2 = \frac{V_2}{R_2}$$

$$I_2 = \frac{120}{200}$$

$$I_2 = 0.6 \text{ A}$$

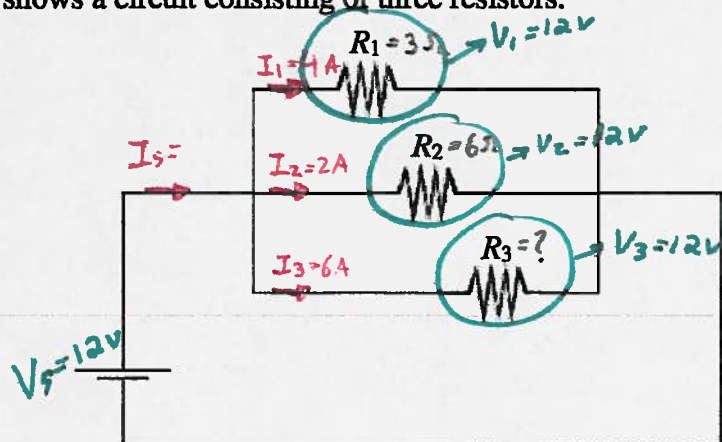12) The following diagram shows a circuit consisting of three resistors.



a) Place the following information on the above circuit diagram:

$$\begin{array}{l} R_1 = 3 \Omega \\ I_1 = 4 \text{ A} \end{array}$$

$$\begin{array}{l} R_2 = 6 \Omega \\ I_2 = 2 \text{ A} \end{array}$$

$$\begin{array}{l} R_3 = ? \\ I_3 = 6 \text{ A} \end{array}$$

b) What is the total current provided by the power source (I_s)? $I_s = I_1 + I_2 + I_3$

(Parallel)
 $I_s = 4 + 2 + 6$
 $I_s = 12 \text{ A}$

c) What is the potential difference of the Power Source (V_s)?

① $V_1 = I_1 R_1$ $V_1 = 12 \text{ V}$
 $V_1 = 4(3)$
 ② $V_s = V_1 = V_2 = V_3$
 (Parallel)
 $V_s = 12 \text{ V}$

d) What is the value of resistor R_3 ?

$$R_3 = \frac{V_3}{I_3} \quad R_3 = \frac{12}{6} = \underline{2 \Omega}$$

Solutions:

- 1) a) 120 V b) 120 V c) 2 A d) 40 Ω e) 60 Ω f) 24 Ω g) 12 Ω
- 2) a) $R_{eq} = 15.79 \Omega$ b) $R_{eq} = 11.67 \Omega$
- 3) a) 1.05 A b) 0.5A c) 1.33A
- 4) 1.5A
- 5) a) $V_1 = 3.5 \text{ V}$ $V_2 = 3.5 \text{ V}$ b) 10V
- 6) 10A
- 7) 3.33A
- 8) 3A
- 9) 1V
- 10) 120V
- 11) a) 40 Ω b) 3A c) 2.4A d) 0.6A
- 12) a) - b) 12A c) 12V d) 2 Ω