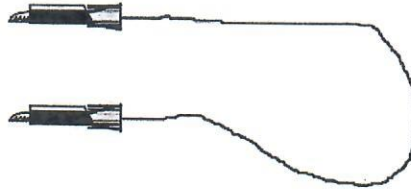


# Practice Problems A

1. Alligator clips are used to connect the components of an electric circuit.



Which substance can be used to make the jaws of these alligator clips?

- a) Aluminum                      c) Plastic  
b) Rubber                              d) Porcelain

2. Porcelain is used to support electrical wires on poles.


Which properties of porcelain make it desirable for this use?

1. Is a good insulator.
2. Is non-ductile.
3. It rusts.
4. Breaks easily.

- a) 1 and 2                              c) 2 and 4  
b) 1 and 3                              d) 3 and 4


3. The four conductors shown below are made out of copper.

Which one has the greatest conductance?

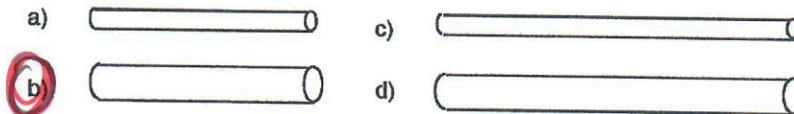

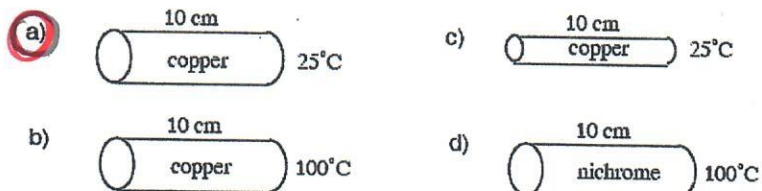4. Several factors can influence the electrical conductivity of a wire.

Which of the following diagrams shows the wire with the best electrical conductivity?




5. Which of the following would increase the conductivity of a circuit ?

- 1 - A thicker wire
- 2 - A longer wire
- 3 - A decrease in the temperature of the wire
- 4 - The use of porcelain wire


- a) 1 and 2    **b) 1 and 3**    c) 2 and 4    d) 3 and 4

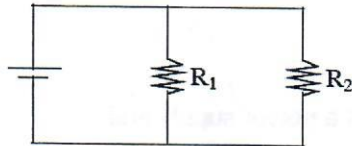6. The diagram of a parallel electric circuit is shown below.




You have to connect ammeter (A) into this circuit so that you will be able to read the total current flowing through resistors  $R_1$  and  $R_2$ .

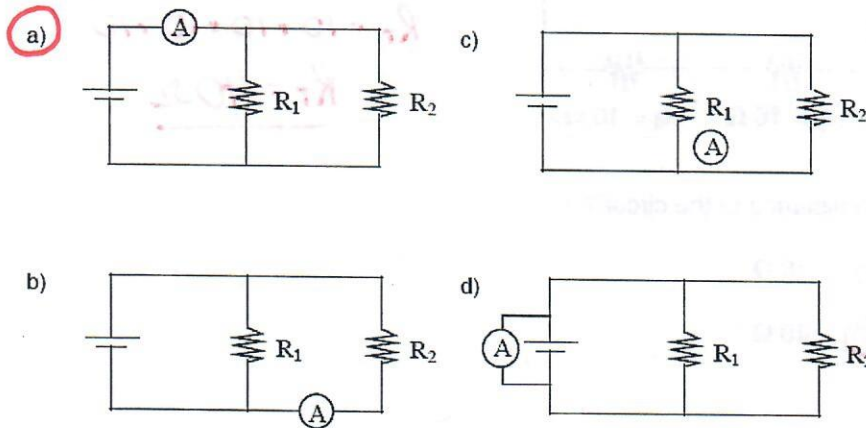Which diagram shows the right way to connect the ammeter?



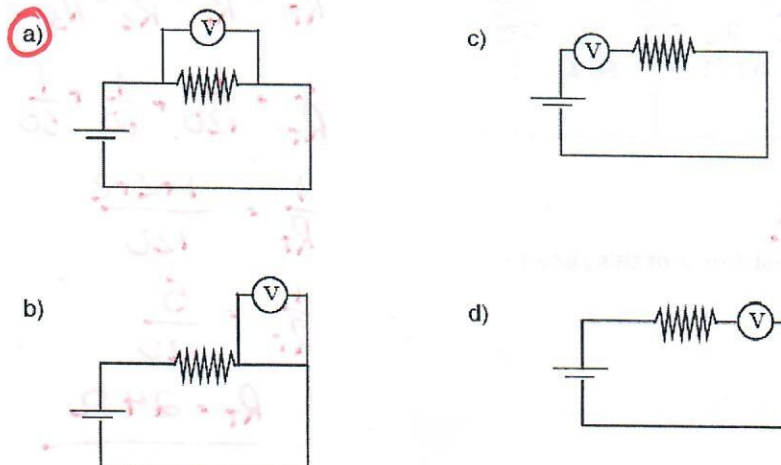
7. You have to connect a voltmeter to determine the potential difference across the terminals of a resistor in a simple circuit.

In which diagram below is the voltmeter properly connected?



## Practice Problems B

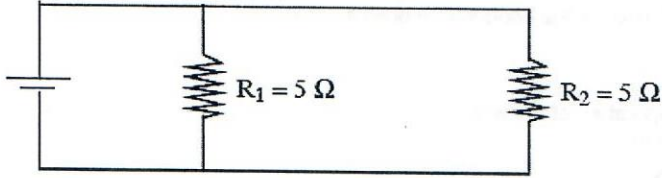1. A parallel circuit is illustrated below.



What is the equivalent resistance of this circuit?

- a) 0.4 Ω      c) 5 Ω  
**b) 2.5 Ω**      d) 10 Ω

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{5} + \frac{1}{5}$$


$$\frac{1}{R_T} = \frac{1+1}{5}$$

$$\frac{1}{R_T} = \frac{2}{5}$$

$$\underline{R_T = 2.5 \Omega}$$

2. The electric circuit illustrated below consists of a power supply and resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .

Series

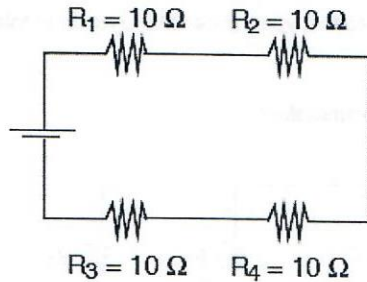

$$R_T = R_1 + R_2 + R_3 + R_4$$


$$R_T = 10 + 10 + 10 + 10$$

$$\underline{R_T = 40 \Omega}$$

What is the equivalent resistance of the circuit?

- a) 0.4 Ω      c) 10 Ω  
 b) 2.5 Ω      **d) 40 Ω**

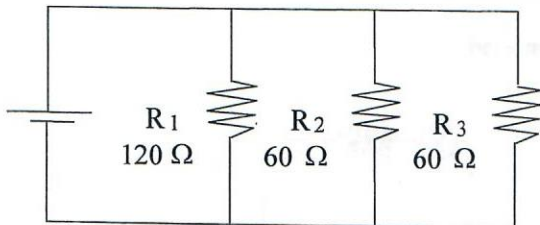3. The circuit illustrated below consists of three resistors ( $R_1$ ,  $R_2$  and  $R_3$ ) and a power supply.



Parallel

What is the equivalent resistance of this circuit?

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{120} + \frac{1}{60} + \frac{1}{60}$$

$$\frac{1}{R_T} = \frac{1+2+2}{120}$$

$$\frac{1}{R_T} = \frac{5}{120}$$


$$\underline{R_T = 24 \Omega}$$

# Practice Problems C

## Equivalent Resistance: Combined Circuits:

Show All Work:

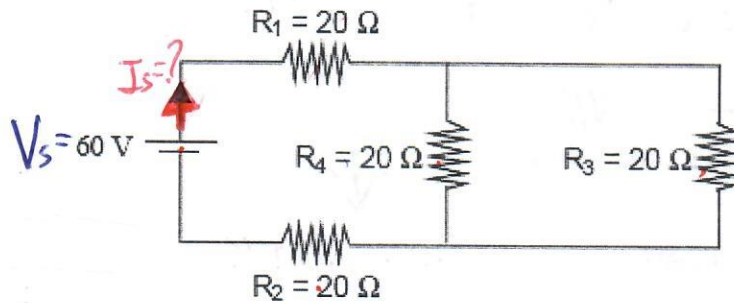- 1) The electric circuit illustrated below consists of a power supply and resistors R1, R2, R3, and R4.



$R_3$  &  $R_4$  are in parallel


- a) What is the total resistance of this circuit?  
 b) What is the current provided by the source?

① step 1

$$\frac{1}{R_{34}} = \frac{1}{R_3} + \frac{1}{R_4}$$

$$\frac{1}{R_{34}} = \frac{1}{20} + \frac{1}{20}$$

$$R_{34} = 10 \Omega$$

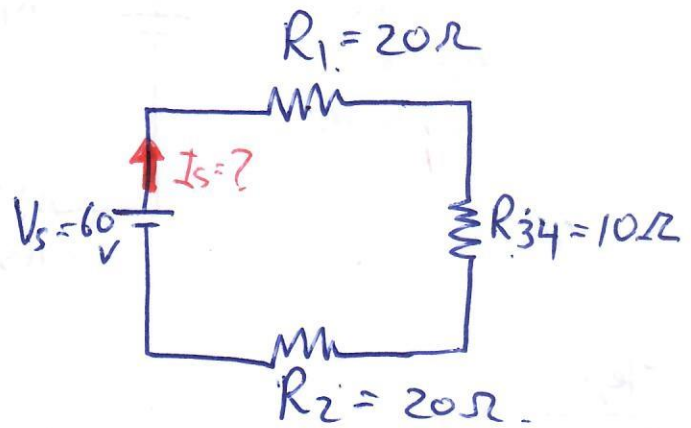

step 2

$$R_T = R_1 + R_2 + R_{34}$$

(series)

$$R_T = 20 + 20 + 10$$


$$R_T = 50 \Omega$$

b)  $R_T = \frac{V_s}{I_s}$

$$I_s = \frac{V_s}{R_T} \quad I_s = \frac{60}{50} = \underline{\underline{1.2 A}}$$






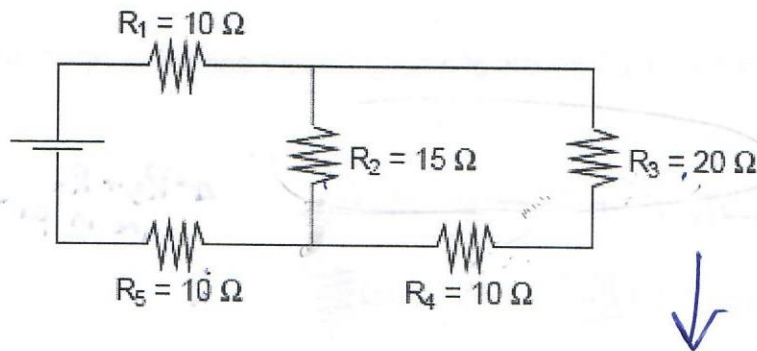2) A series-parallel electric circuit is illustrated below.



What is the equivalent resistance of this circuit?

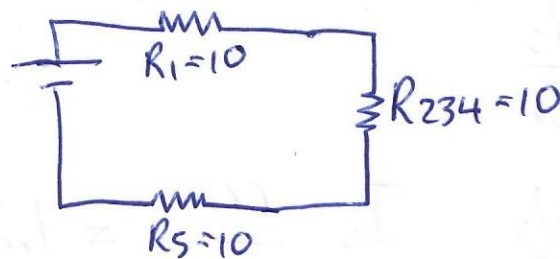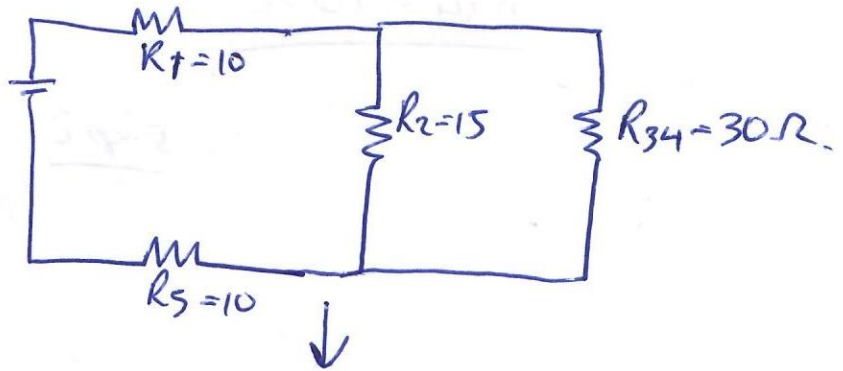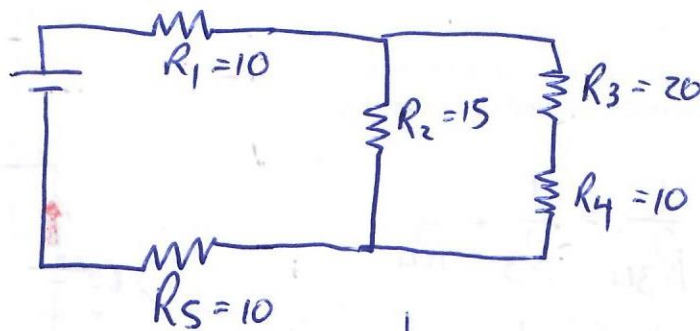- a) 2.4 Ω
- b) 24.6 Ω
- c) 30.0 Ω**
- d) 65.0 Ω



step 1

$$R_{34} = R_3 + R_4$$

series

$$R_{34} = 20 + 10$$

$$\underline{R_{34} = 30 \Omega}$$

step 2

$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_{34}}$$

(parallel)

$$\frac{1}{R_{234}} = \frac{1}{15} + \frac{1}{30}$$

$$\underline{R_{234} = 10 \Omega}$$

step 3:  $R_T = R_1 + R_{234} + R_5$   
 (series)  $R_T = 10 + 10 + 10$   
 $\underline{R_T = 30 \Omega}$