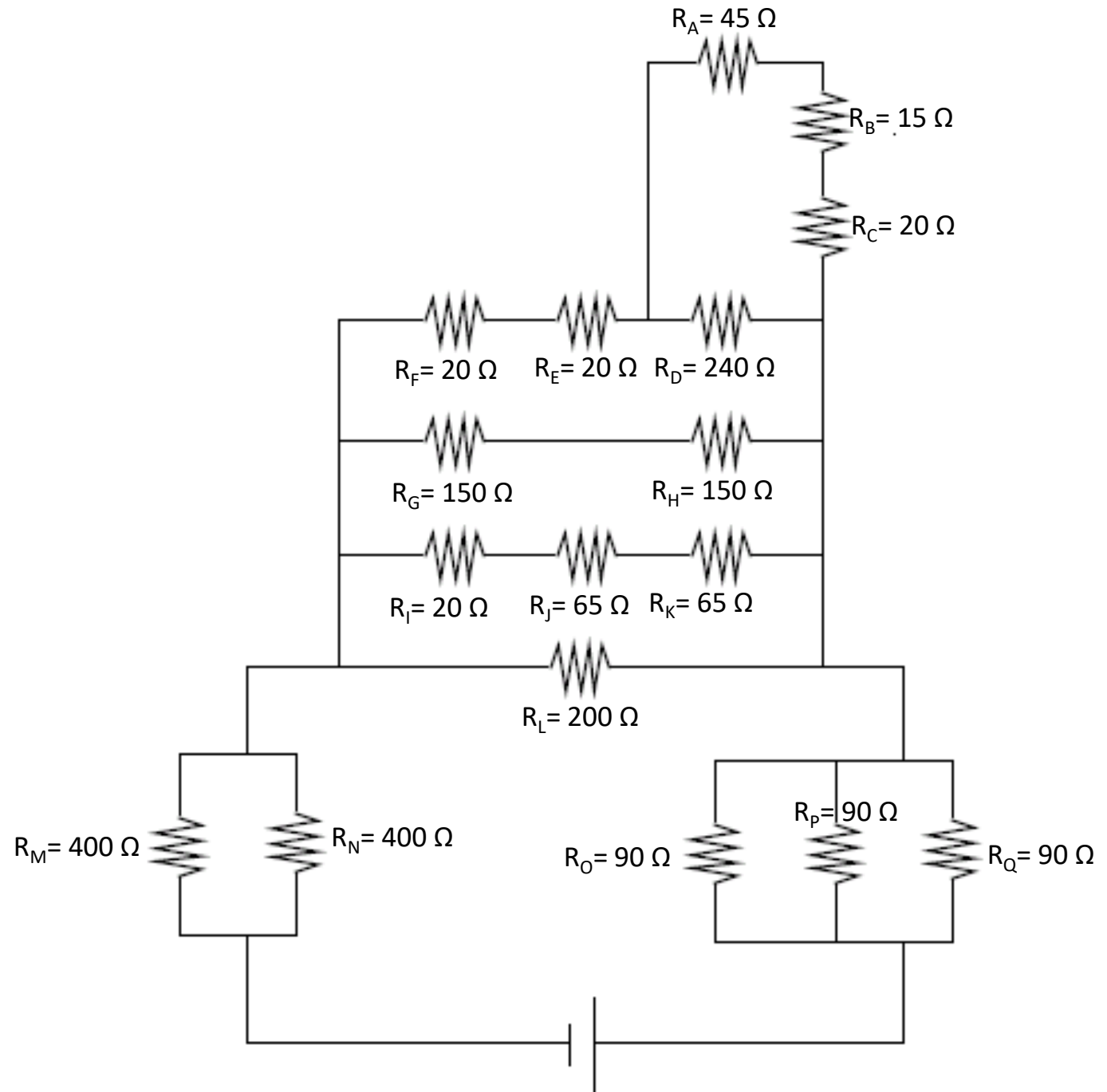


# Equivalent Resistance Challenge !!!

Solve for  $R_{eq}$




**STEP 1:**

**Series**

$$R_{ABC} = R_A + R_B + R_C$$

$$R_{ABC} = 45 + 15 + 20$$

$$R_{ABC} = 80 \Omega$$

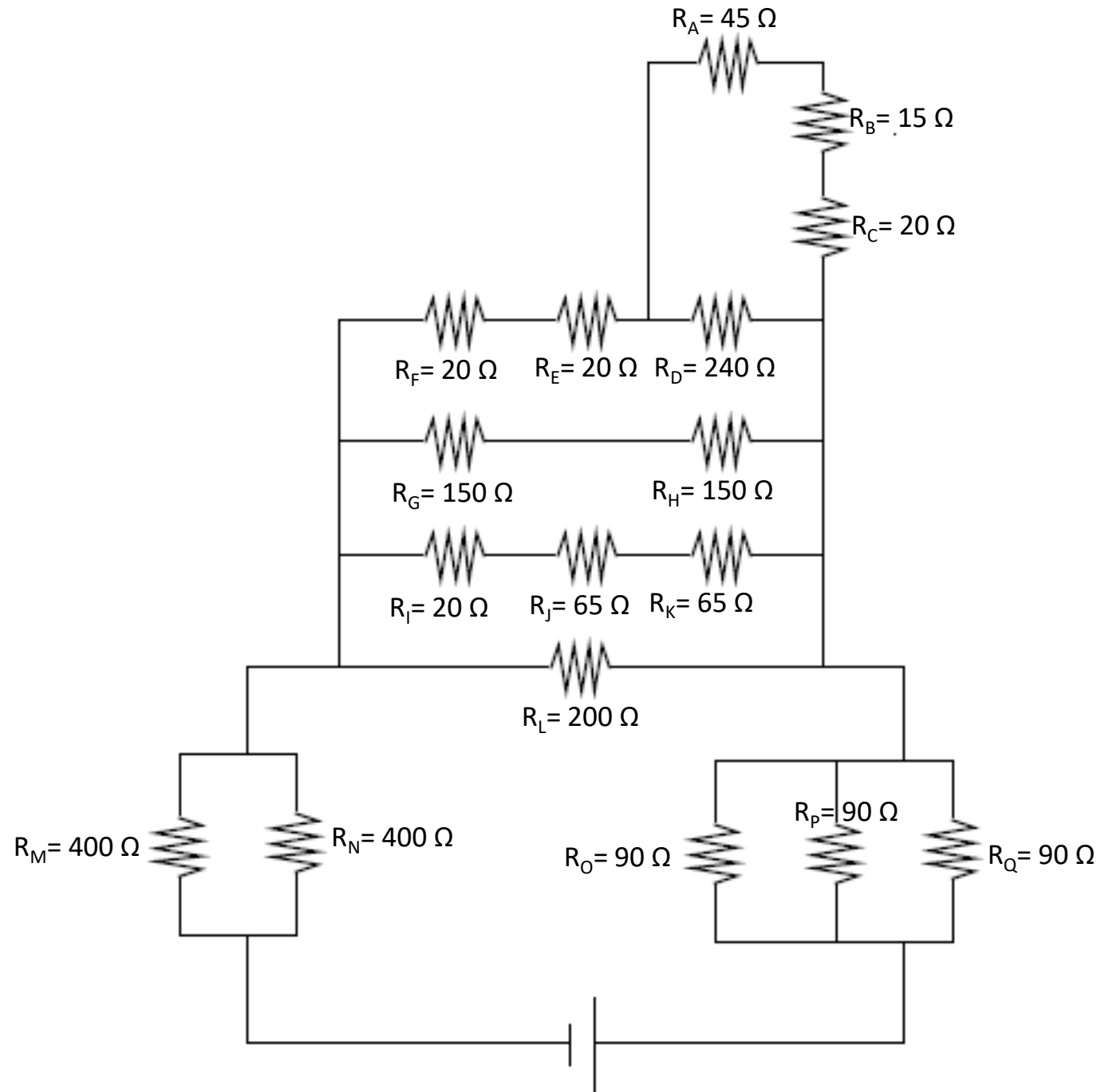


**STEP 2:**

**PARALLEL**

$$1/R_{ABCD} = 1/R_{ABC} + 1/R_{ABC}$$

$$1/R_{ABCD} = 1/80 + 1/240$$

$$R_{ABCD} = 60 \Omega$$

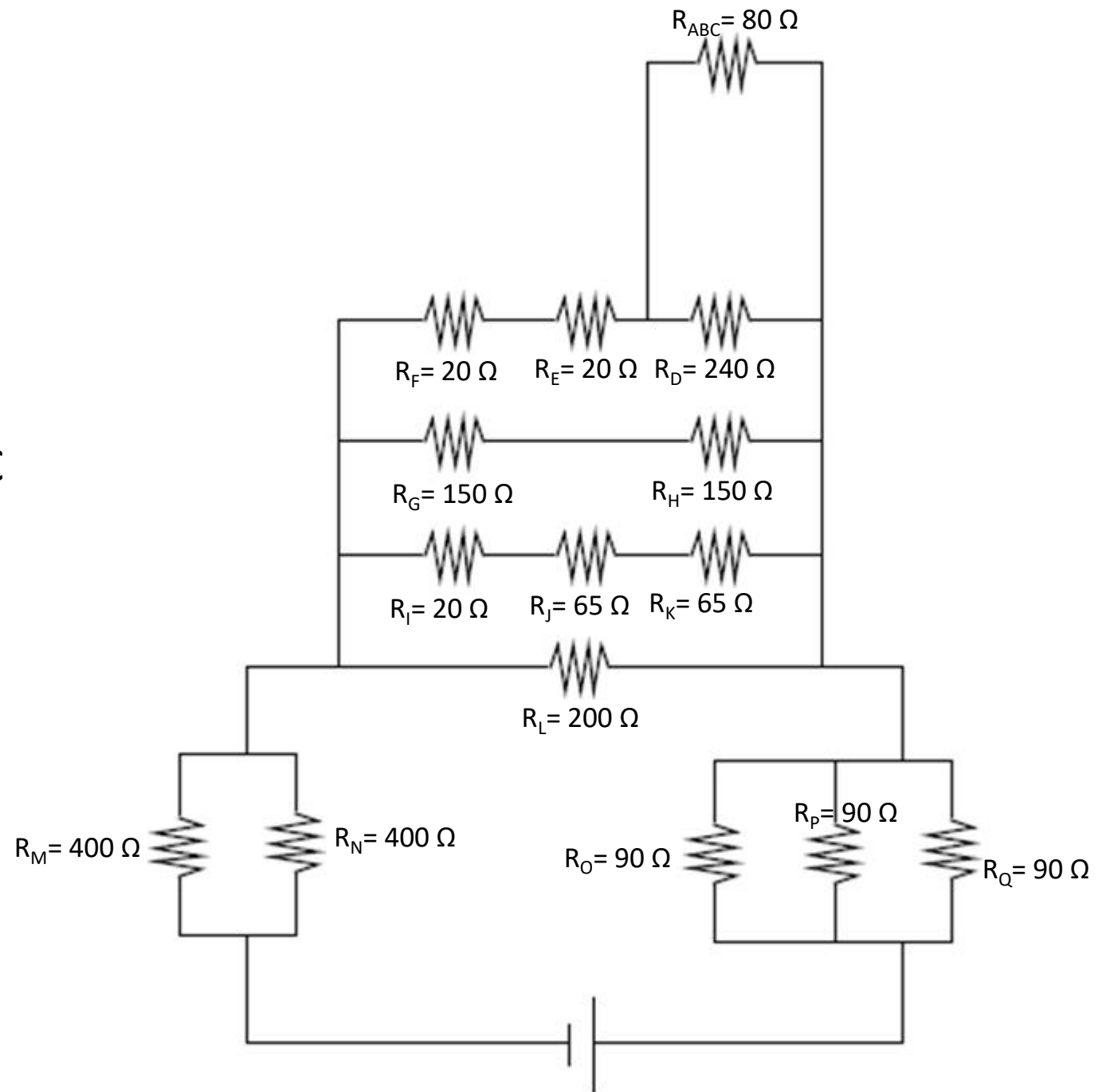


**STEP 3:**

**SERIES**

$$R_{A-F} = R_{ABCD} + R_E + R_F$$

$$R_{A-F} = 60 + 20 + 20$$

$$R_{A-F} = 100 \Omega$$

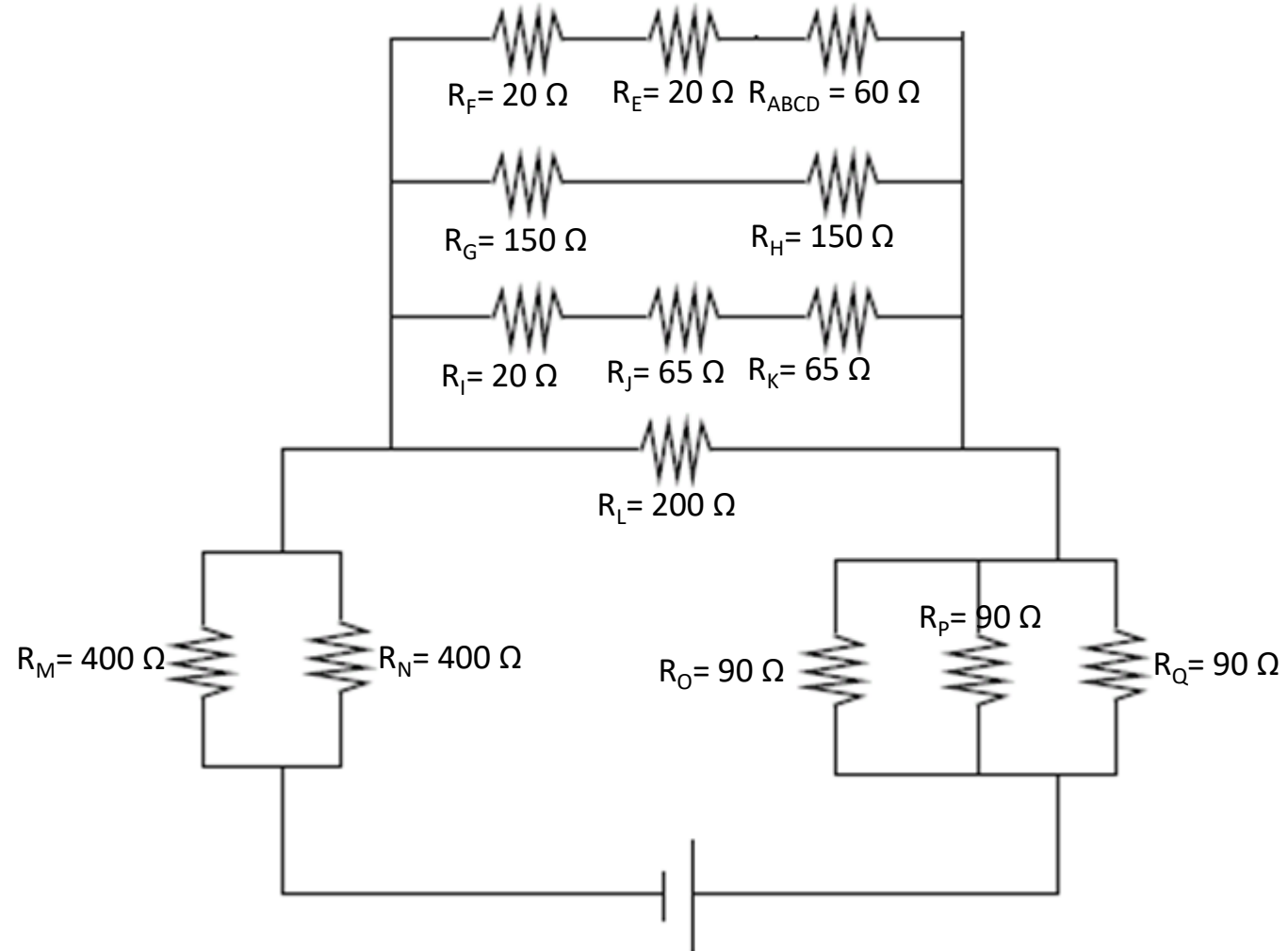


**STEP 4:**

**SERIES**

$$R_{GH} = R_G + R_H$$

$$R_{GH} = 150 + 150$$

$$R_{GH} = 300 \Omega$$

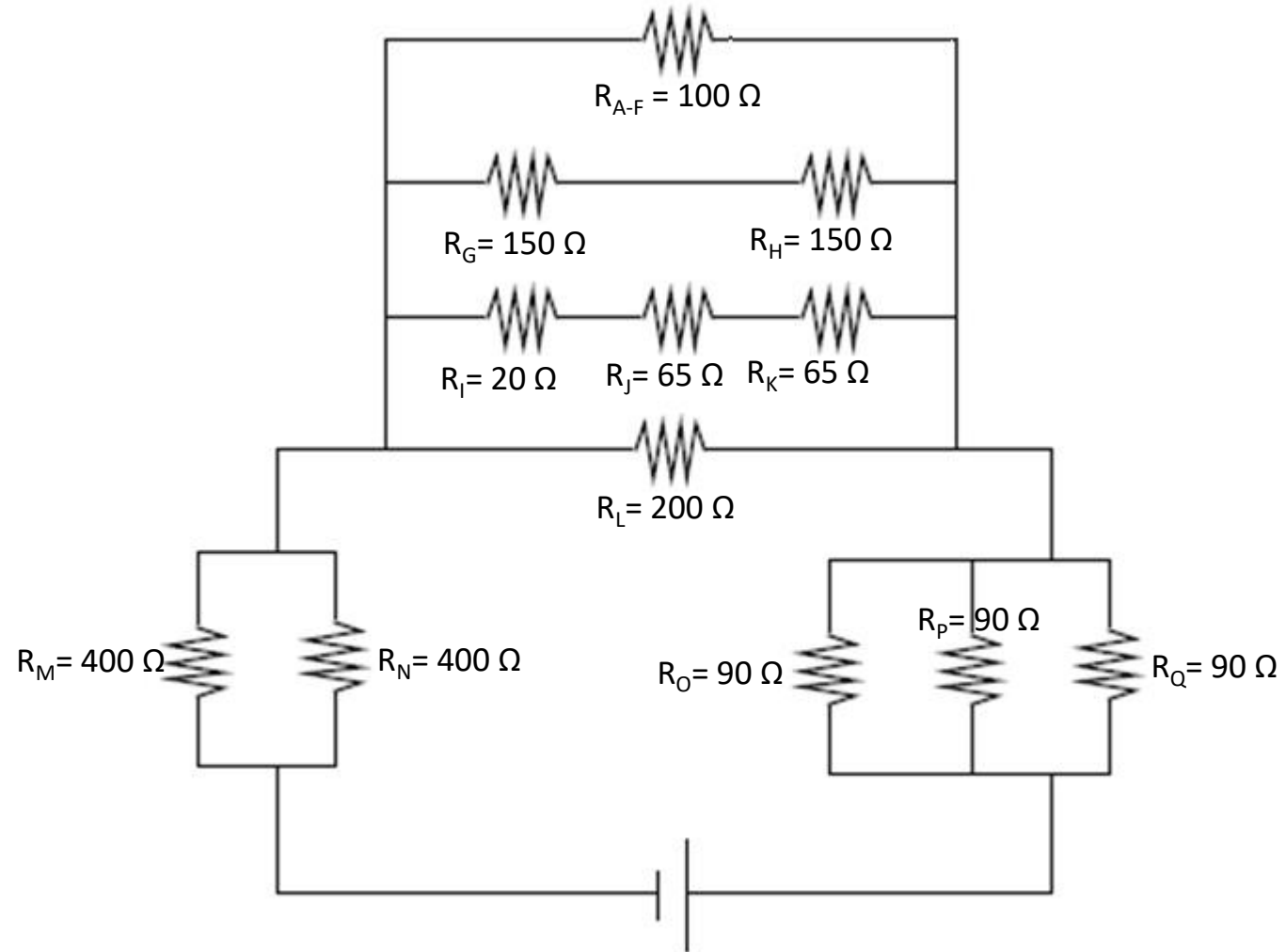


**STEP 5:**

**SERIES**

$$R_{IJK} = R_I + R_J + R_K$$

$$R_{IJK} = 20 + 65 + 65$$

$$R_{IJK} = 150 \Omega$$

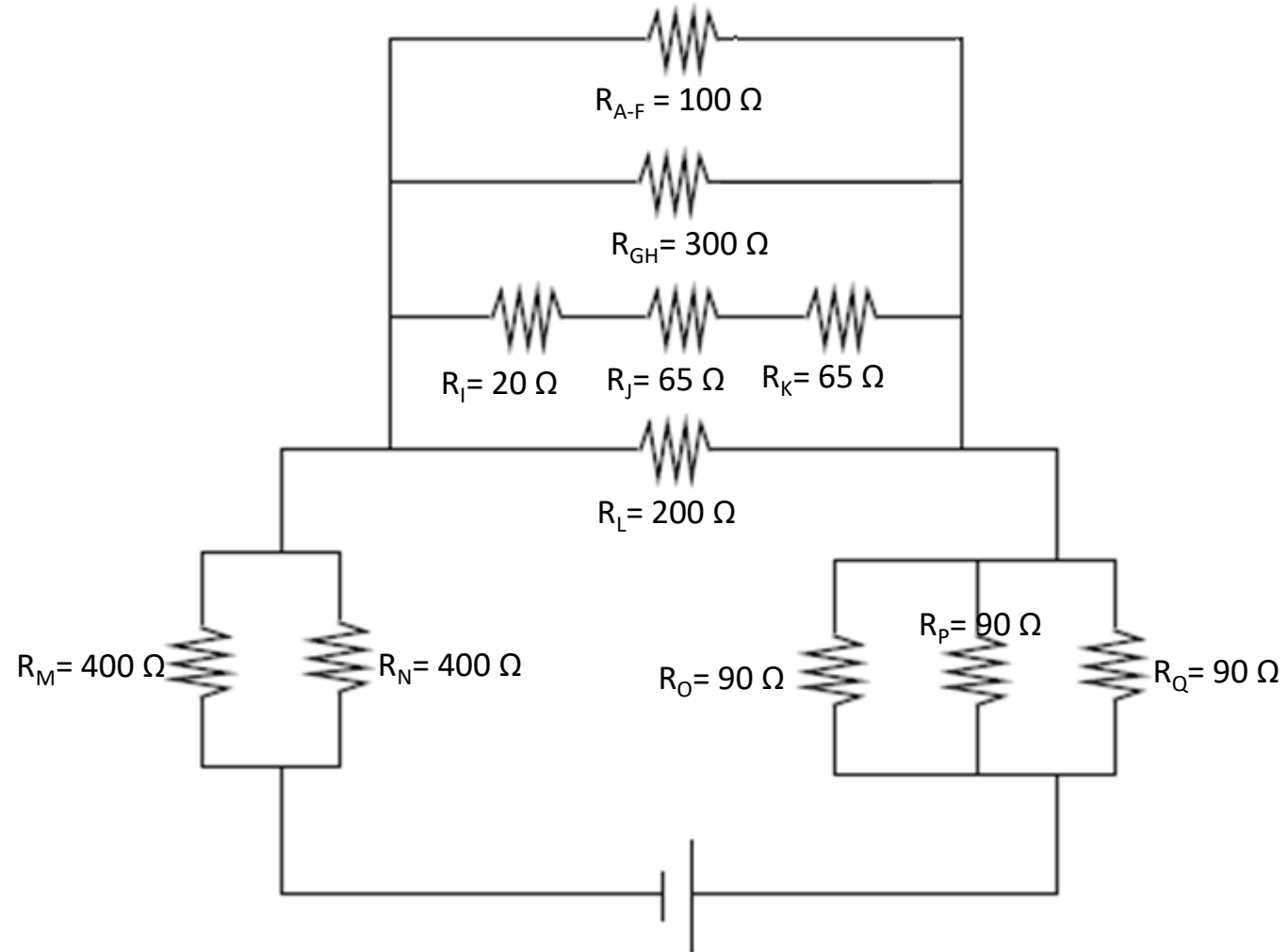

**STEP 6:**


**PARALLEL**

$$1/R_{A-L} = 1/R_{A-F} + 1/R_{GH} + 1/R_{IJK} + 1/R_L$$

$$1/R_{A-L} = 1/100 + 1/300 + 1/150 + 1/200$$

$$1/R_{A-L} = (6+2+4+3)/600$$

$$R_{A-L} = 40 \Omega$$

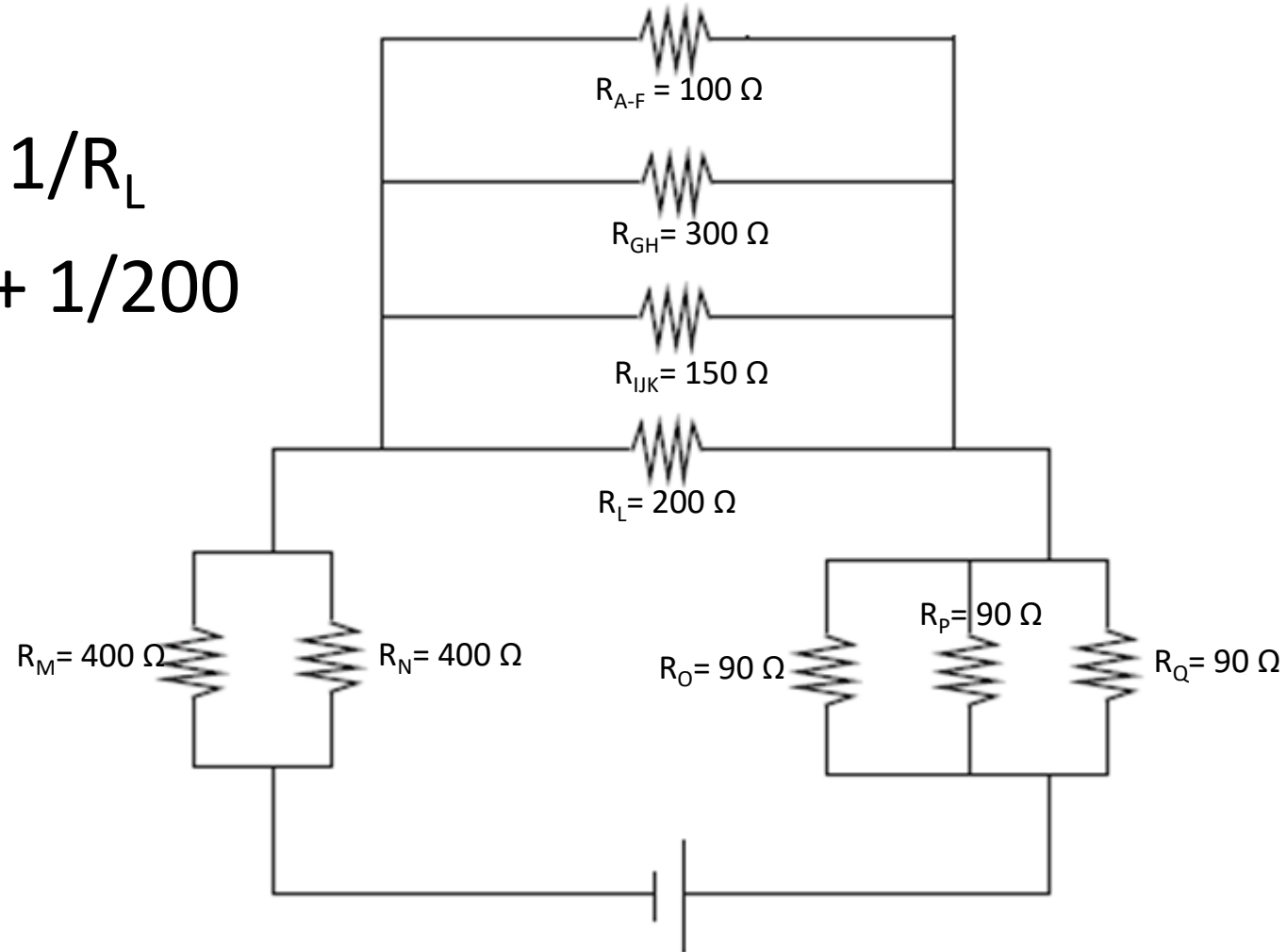


**STEP 7:**

**PARALLEL**

$$1/R_{MN} = 1/R_M + 1/R_N$$

$$1/R_{MN} = 1/400 + 1/400$$

$$R_{MN} = 200 \Omega$$

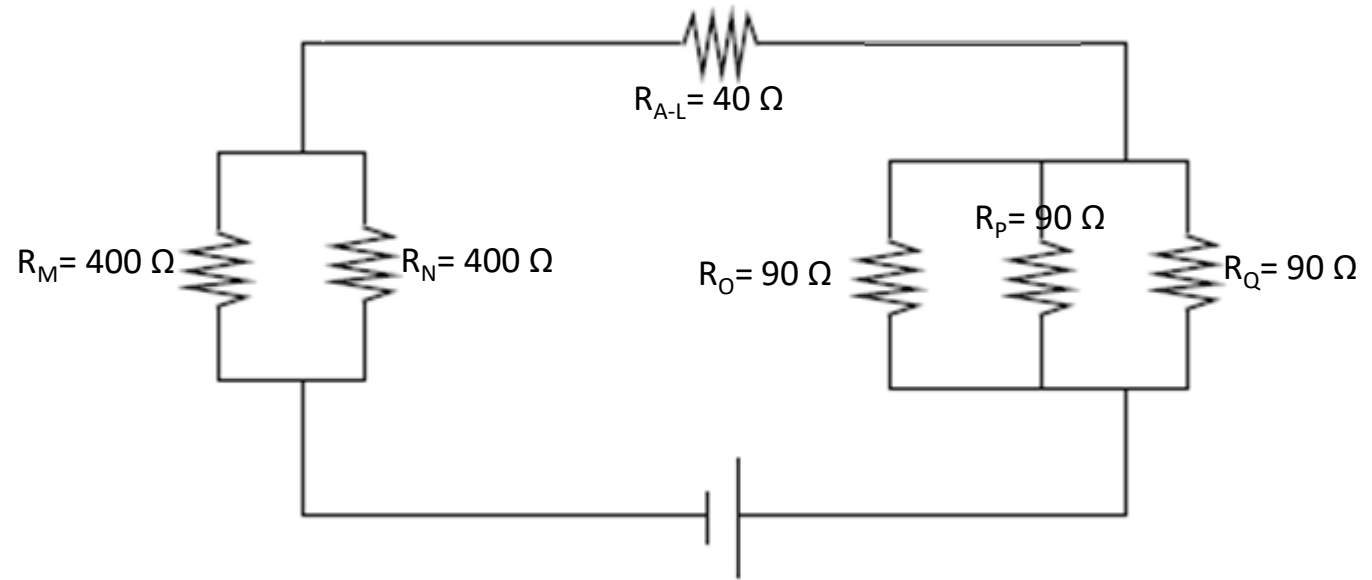




**STEP 8:**

**PARALLEL**

$$1/R_{OPQ} = 1/R_O + 1/R_P + 1/R_Q$$

$$1/R_{OPQ} = 1/90 + 1/90 + 1/90$$

$$R_{OPQ} = 30 \Omega$$

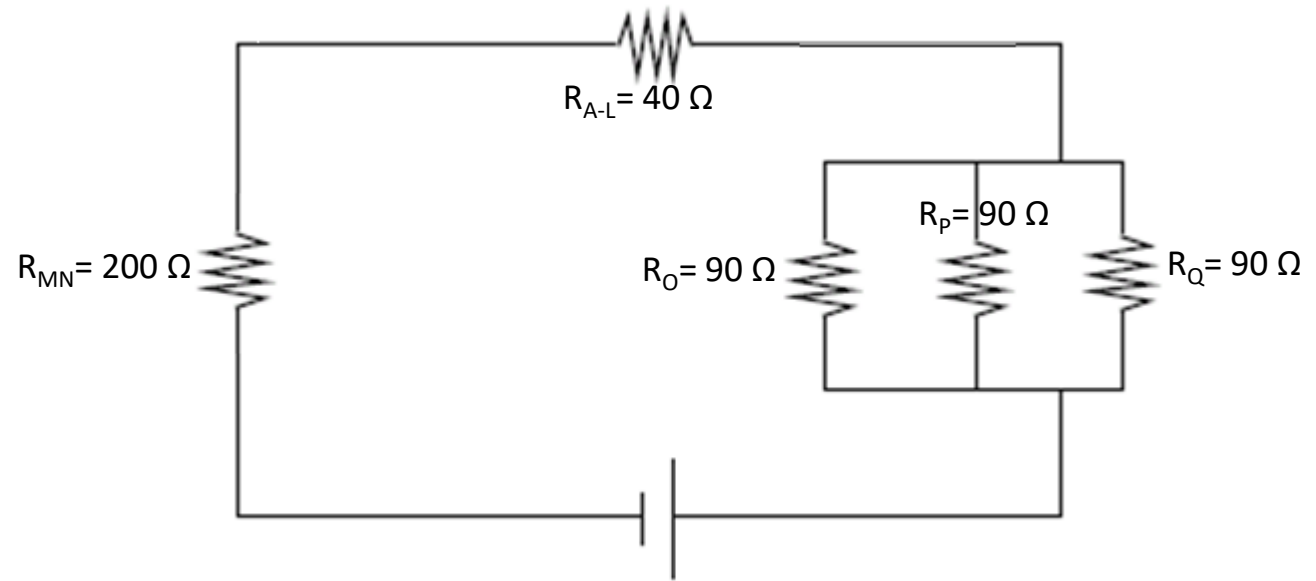

**STEP 9:**

**SERIES**

$$R_T = 1/R_{A-L} + 1/R_{MN} + 1/R_{OPQ}$$

$$R_T = 40 + 200 + 30$$

$$\underline{\underline{R_T = 270 \Omega}}$$

