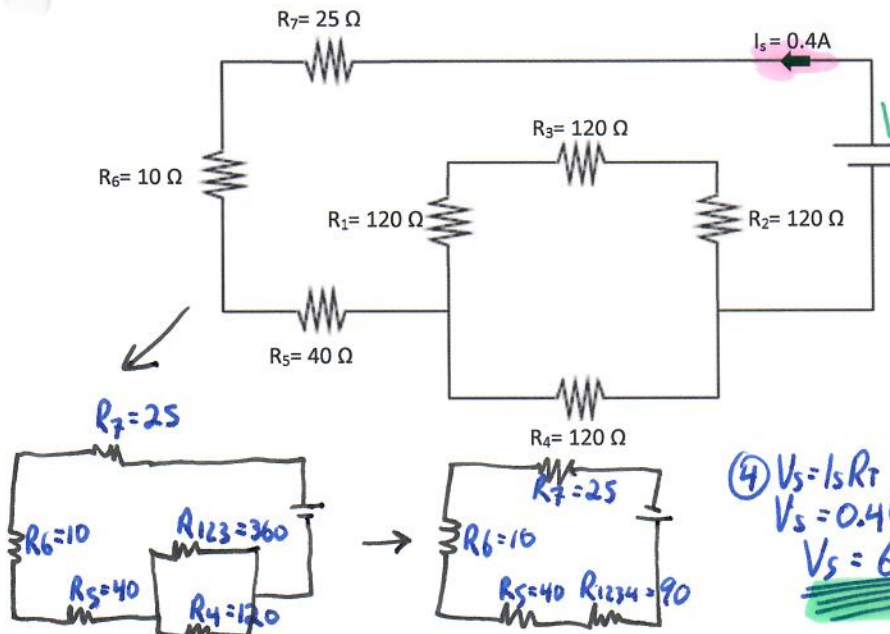


Practice Quiz: Resistance & Equivalent Resistance

name: SOLUTIONS

1) Calculate the Potential Difference of the power source.




① $R_{123} = R_1 + R_2 + R_3$
 $R_{123} = 120 + 120 + 120$
 $R_{123} = 360 \Omega$

② $\frac{1}{R_{1234}} = \frac{1}{R_{123}} + \frac{1}{R_4}$
 $\frac{1}{R_{1234}} = \frac{1}{360} + \frac{1}{120}$
 $R_{1234} = 90 \Omega$

③ $R_T = R_{1234} + R_5 + R_6 + R_7$
 $R_T = 90 + 40 + 10 + 25$
 $R_T = 165 \Omega$

④ $V_s = I_s R_T$
 $V_s = 0.4 (165)$
 $V_s = 66V$

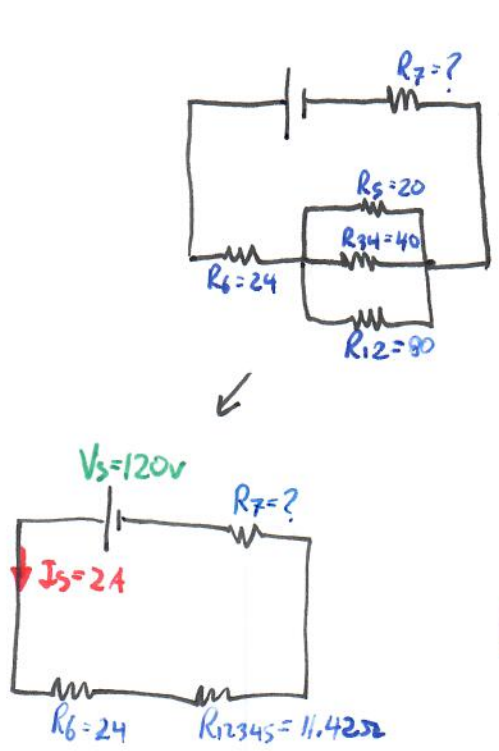
2) Given the information in the diagram, calculate the value of resistor R_7



③ $\frac{1}{R_{12345}} = \frac{1}{R_{12}} + \frac{1}{R_{34}} + \frac{1}{R_5}$
 $\frac{1}{R_{12345}} = \frac{1}{80} + \frac{1}{40} + \frac{1}{20}$
 $R_{12345} = 11.42$

④ $R_T = \frac{V_s}{I_s}$
 $R_T = \frac{120}{2}$
 $R_T = 60 \Omega$

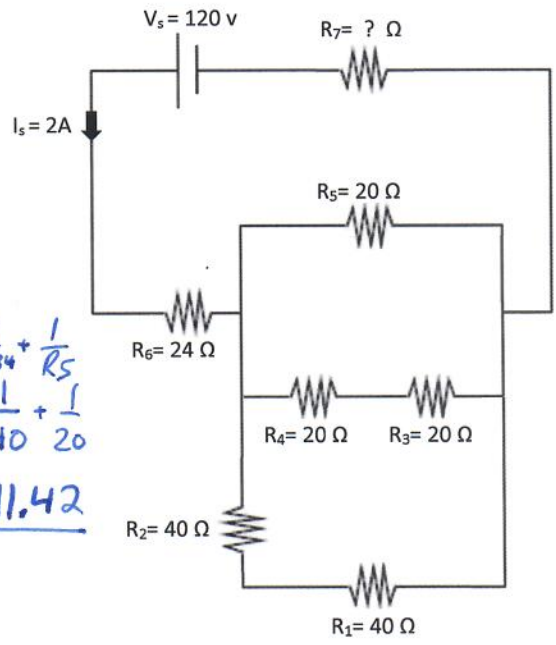⑤ $R_T = R_{12345} + R_6 + R_7$
 $60 = 11.42 + 24 + R_7$
 $R_7 = 24.6 \Omega$



① $R_{12} = R_1 + R_2$
 $R_{12} = 40 + 40$
 $R_{12} = 80 \Omega$

② $R_{34} = R_3 + R_4$
 $R_{34} = 20 + 20$
 $R_{34} = 40 \Omega$