

Resistance & Equivalent Resistance:

name: SOLUTIONS

- 1) An automobile starter requires 100 Amps of current and a 12 V battery. What is the Resistance of the starter ?

$$R = \frac{V}{I}$$

$$R = \frac{12}{100}$$

$$\underline{R = 0.12 \Omega}$$


- 2) What potential difference is required for a 0.05 A current to flow through a 1500 Ω resistor ?

$$V = IR$$

$$V = 0.05(1500)$$


$$\underline{V = 75V}$$

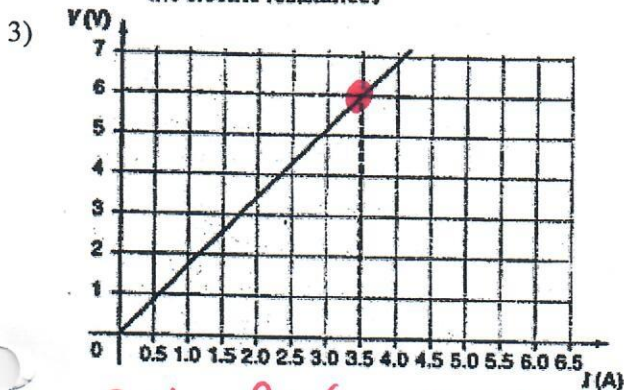Using the following $V = f(I)$ graph, determine the electric resistance.




$$R = \frac{V}{I} \quad R = \frac{6}{3.5} \quad \underline{R = 1.75 \Omega}$$

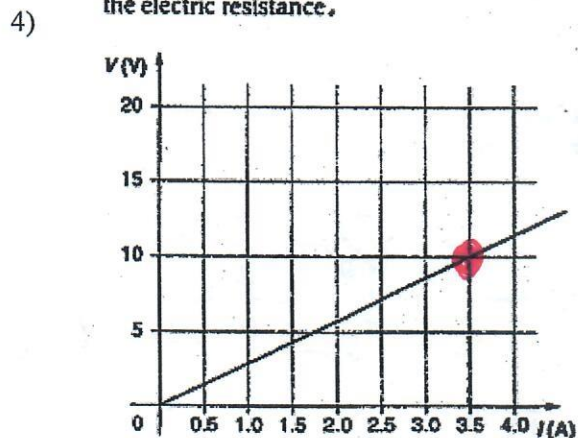Using the following $V = f(I)$ graph, determine the electric resistance.



$$R = \frac{V}{I} \quad R = \frac{10}{3.5} \quad \underline{R = 2.85 \Omega}$$

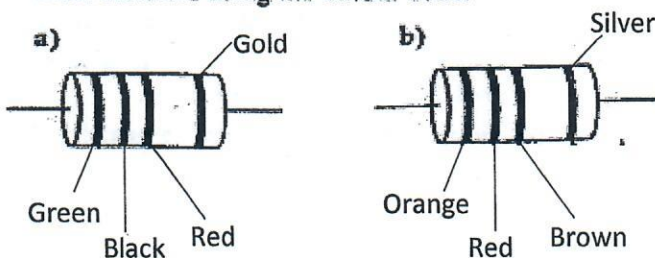- 5) Determine the electric resistance and tolerance of these resistors using the colour code.





a) $50 \times 10^2 \Omega \pm 5\%$
 $\underline{5000 \Omega \pm 5\%}$

b) $32 \times 10^1 \Omega \pm 10\%$
 $\underline{320 \Omega \pm 10\%}$

Range:
 $5000 \Omega \pm 250 \Omega$
 $\underline{4750 \text{ to } 5250 \Omega}$

Range:
 $320 \Omega \pm 32 \Omega$
 $\underline{288 \text{ to } 352 \Omega}$

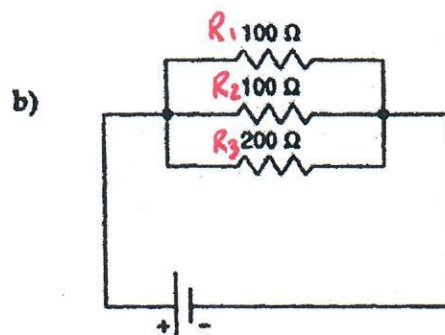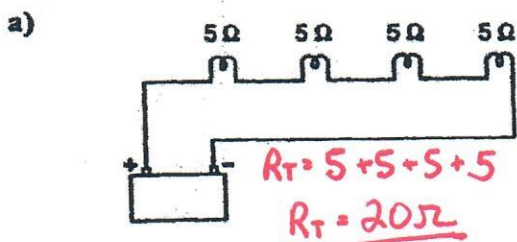- 6) Determine the equivalent resistance of each of the following circuits:



$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{100} + \frac{1}{100} + \frac{1}{200}$$


$$\frac{1}{R_T} = \frac{2+2+1}{200}$$

$$\frac{1}{R_T} = \frac{5}{200}$$

$$\underline{R_T = 40 \Omega}$$

- 7) Calculate the equivalent resistance of each of the following combination circuits.

a)

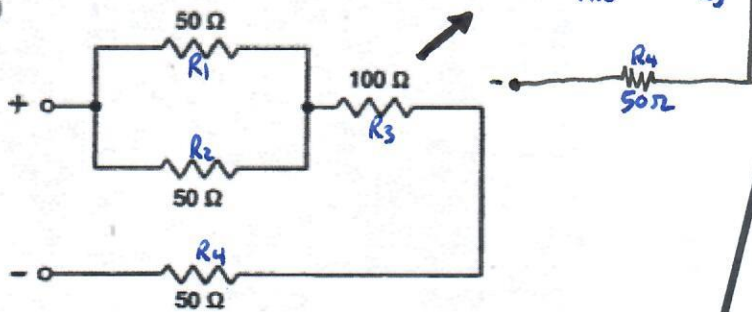


$$\begin{aligned} \textcircled{1} \frac{1}{R_{12}} &= \frac{1}{R_1} + \frac{1}{R_2} \\ \frac{1}{R_{12}} &= \frac{1}{50} + \frac{1}{50} \\ R_{12} &= 25 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} R_T &= R_{12} + R_3 + R_4 \text{ series} \\ R_T &= 25 + 100 + 50 \\ R_T &= 175 \Omega \end{aligned}$$

- 8) Calculate the current coming from the batteries in the following circuits.


a)

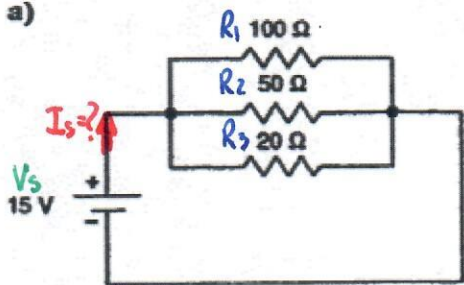

$$\begin{aligned} \textcircled{1} \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ \frac{1}{R_T} &= \frac{1}{100} + \frac{1}{50} + \frac{1}{20} \\ \frac{1}{R_T} &= \frac{1+2+5}{100} \\ R_T &= 12.5 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} I_s &= \frac{V_s}{R_T} \\ I_s &= \frac{15}{12.5} \\ I_s &= 1.2 \text{ A} \end{aligned}$$


b)

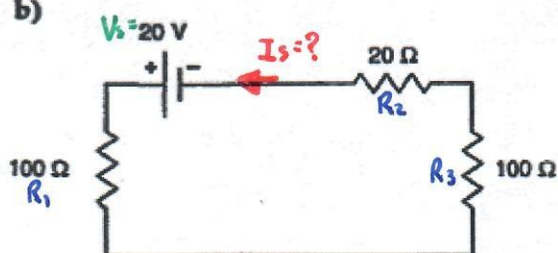

$$\begin{aligned} \textcircled{1} R_T &= R_1 + R_2 + R_3 \\ R_T &= 100 + 20 + 100 \\ R_T &= 220 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} I_s &= \frac{V_s}{R_T} \\ I_s &= \frac{20}{220} = 0.09 \text{ A} \end{aligned}$$

b)

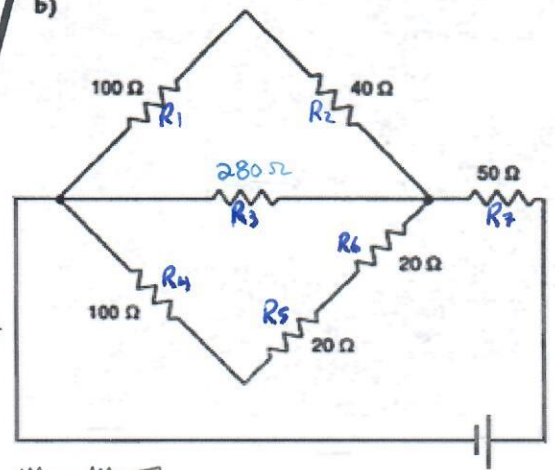

$$\begin{aligned} \textcircled{1} & \text{Circuit diagram showing R1, R2, R3, R4, R5, R6 in parallel, then R7 in series.} \\ \textcircled{2} R_{12} &= R_1 + R_2 \\ R_{12} &= 100 + 40 \\ R_{12} &= 140 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{3} R_{456} &= R_4 + R_5 + R_6 \\ R_{456} &= 100 + 20 + 20 \\ R_{456} &= 140 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{4} & \text{Circuit diagram showing R12 (140 ohms) and R3 (280 ohms) in parallel, then R456 (140 ohms) in series.} \end{aligned}$$

$$\begin{aligned} \textcircled{5} \frac{1}{R_{123456}} &= \frac{1}{R_{12}} + \frac{1}{R_3} + \frac{1}{R_{456}} \\ \frac{1}{R_{123456}} &= \frac{1}{140} + \frac{1}{280} + \frac{1}{140} \\ R_{123456} &= 56 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{6} & \text{Circuit diagram showing R123456 (56 ohms) and R7 (50 ohms) in series.} \end{aligned}$$

$$\begin{aligned} \textcircled{7} R_T &= R_{123456} + R_7 \\ R_T &= 56 + 50 \\ R_T &= 106 \Omega \end{aligned}$$

- 9) a) A bulb operating on 110 V is carrying a 0.9 A current. What is the resistance of the bulb?
 b) Determine the equivalent resistance of three such bulbs connected in series.
 c) Determine the equivalent resistance of three such bulbs connected in parallel.

$$\begin{aligned} \text{a) } R &= \frac{V}{I} \\ R &= \frac{110}{0.9} = 122 \Omega \end{aligned}$$


$$\begin{aligned} \text{b) } R_T &= 122 + 122 + 122 \\ R_T &= 366 \Omega \end{aligned}$$

$$\begin{aligned} \text{c) } \frac{1}{R_T} &= \frac{1}{122} + \frac{1}{122} + \frac{1}{122} \\ \frac{1}{R_T} &= \frac{1+1+1}{122} \end{aligned}$$

$$R_T = 40.7 \Omega$$

10) Determine the current leaving the battery in each of the following circuits.

a)

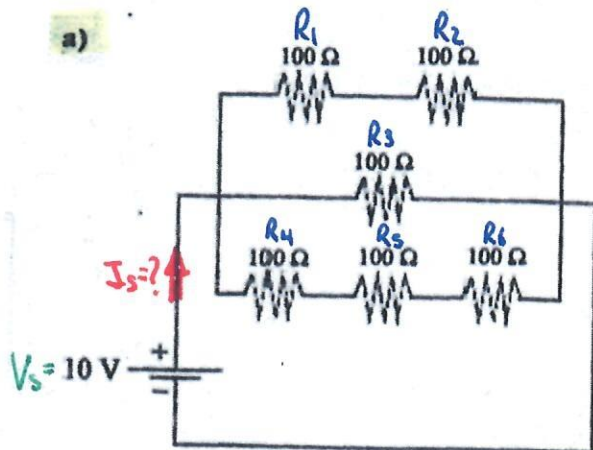

① $R_{12} = R_1 + R_2$
 $R_{12} = 200\Omega$

② $R_{456} = R_4 + R_5 + R_6$
 $R_{456} = 300\Omega$

④ $\frac{1}{R_T} = \frac{1}{R_{12}} + \frac{1}{R_3} + \frac{1}{R_{456}}$

$\frac{1}{R_T} = \frac{1}{200} + \frac{1}{300} + \frac{1}{100}$

$\frac{1}{R_T} = \frac{3+6+2}{600}$

$\frac{1}{R_T} = \frac{11}{600}$

$R_T = 54.5\Omega$

⑤ $I_s = \frac{V_s}{R_T}$

$I_s = \frac{10}{54.5} \quad I_s = 0.18A$

⑤ $R_T = R_1 + R_2 + R_{34567}$
(series)

$R_T = 50 + 100 + 50$

$R_T = 200\Omega$


④ $\frac{1}{R_{34567}} = \frac{1}{R_3} + \frac{1}{R_{4567}}$
(Parallel)

$R_{34567} = 50\Omega$


⑥ $I_s = \frac{V_s}{R_T}$

$I_s = \frac{200}{200}$

$I_s = 1A$

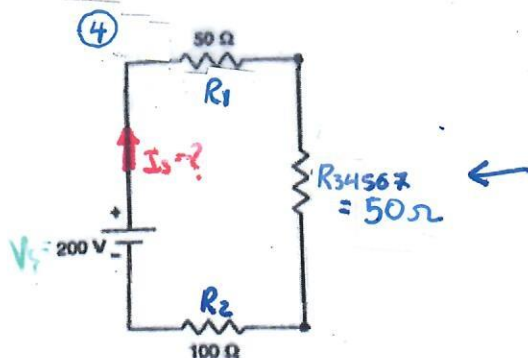

b)

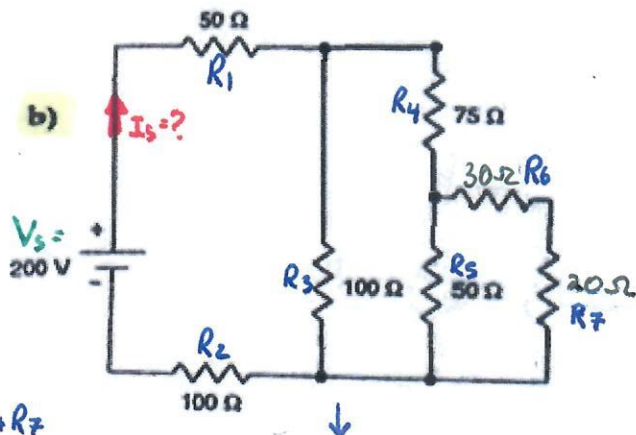

① $R_{67} = R_6 + R_7$
(series)

$R_{67} = 50\Omega$

② $\frac{1}{R_{567}} = \frac{1}{R_5} + \frac{1}{R_67}$
(parallel)




$\frac{1}{R_{567}} = \frac{1}{50} + \frac{1}{50}$

$R_{567} = 25\Omega$

③ $R_{4567} = R_4 + R_{567}$
(series)


$R_{4567} = 75 + 25$

$R_{4567} = 100\Omega$

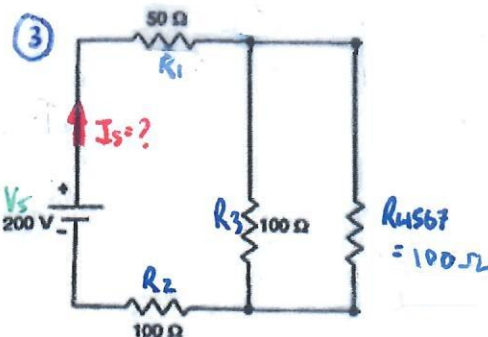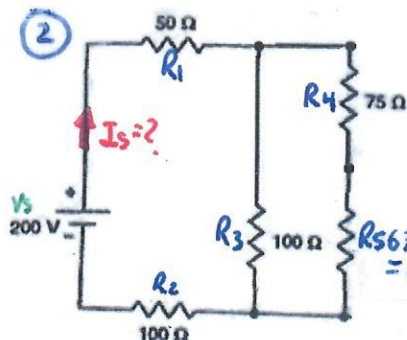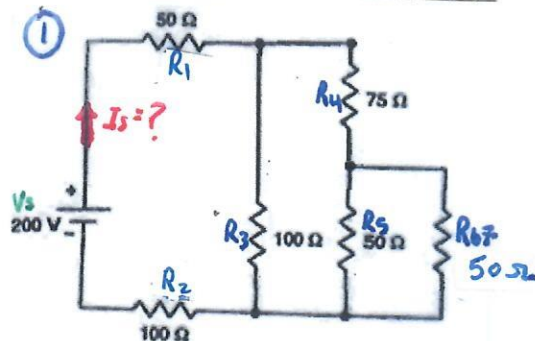

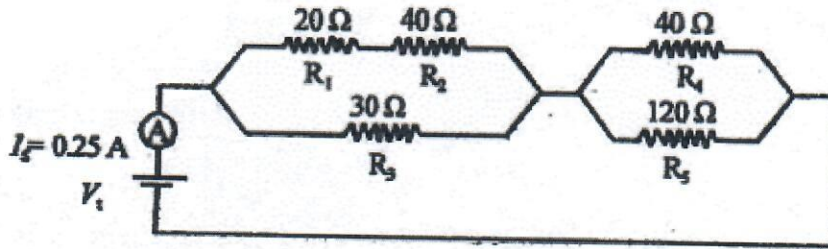
11)

The following electric circuit consists of a power supply, five resistors (R_1 , R_2 , R_3 , R_4 and R_5) and an ammeter A .




What is the potential difference (voltage), V_s , across the power supply?

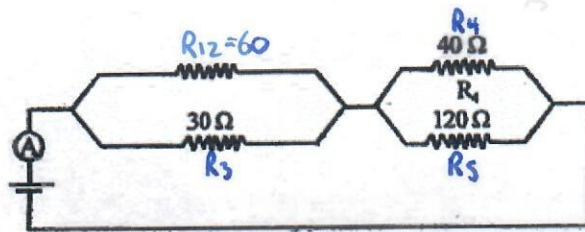① $R_{12} = R_1 + R_2$
 (series)
 $R_{12} = 20 + 40$
 $R_{12} = 60 \Omega$



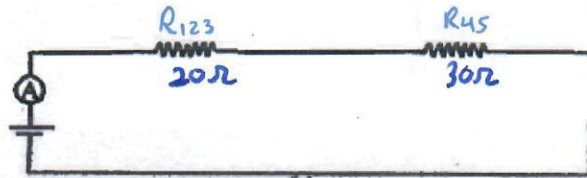② $\frac{1}{R_{123}} = \frac{1}{R_{12}} + \frac{1}{R_3}$
 (parallel)
 $\frac{1}{R_{123}} = \frac{1}{60} + \frac{1}{30}$
 $R_{123} = 20 \Omega$




③ $\frac{1}{R_{45}} = \frac{1}{R_4} + \frac{1}{R_5}$
 (parallel)
 $\frac{1}{R_{45}} = \frac{1}{40} + \frac{1}{120}$
 $R_{45} = 30 \Omega$


④ $R_T = R_{123} + R_{45}$
 series.
 $R_T = 20 + 30$
 $R_T = 50 \Omega$

⑤ $V_s = I_s R_T$
 $V_s = 0.25(50)$
 $V_s = 12.5 \text{ V}$


#12) FIND R_T

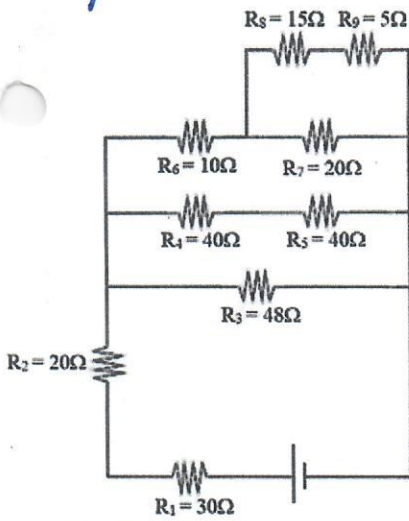

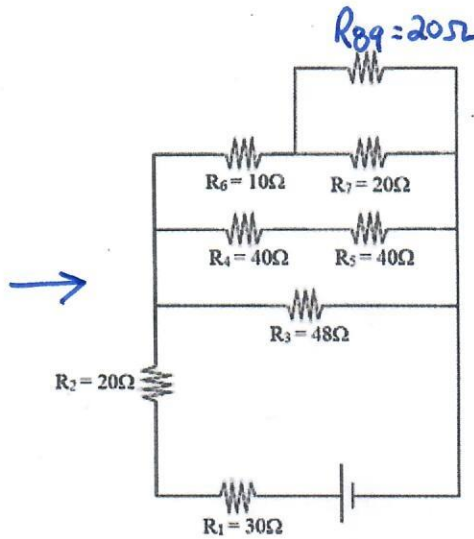
① $R_{89} = R_8 + R_9$
 $R_{89} = 15 + 5$
 $R_{89} = 20\Omega$



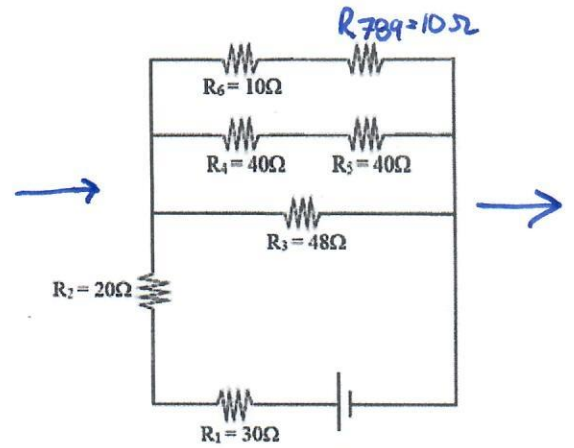
② $\frac{1}{R_{789}} = \frac{1}{R_7} + \frac{1}{R_{89}}$
 $\frac{1}{R_{789}} = \frac{1}{20} + \frac{1}{20}$
 $R_{789} = 10\Omega$



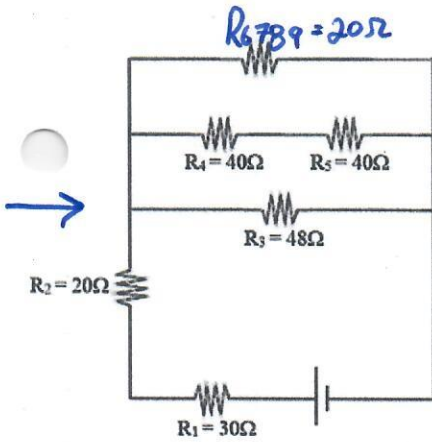
③ $R_{6789} = R_6 + R_{789}$
 $R_{6789} = 10 + 10$
 $R_{6789} = 20\Omega$



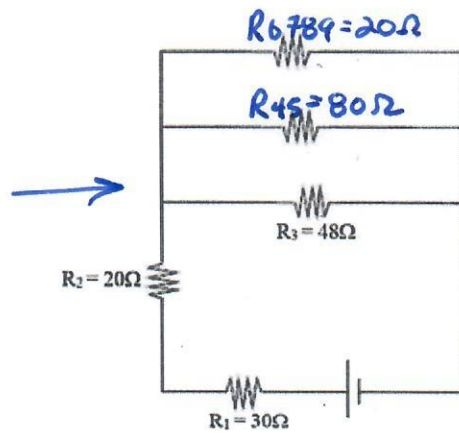④ $R_{45} = R_4 + R_5$
 $R_{45} = 40 + 40$
 $R_{45} = 80\Omega$



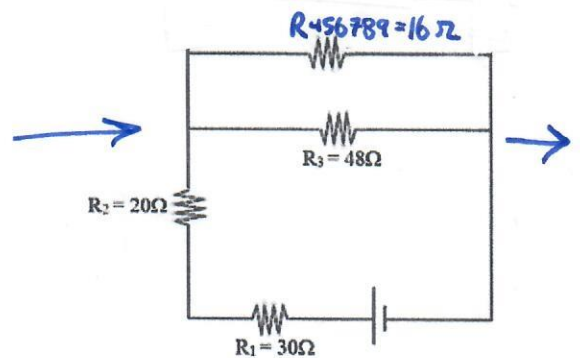
⑤ $\frac{1}{R_{456789}} = \frac{1}{R_{45}} + \frac{1}{R_{6789}}$
 $\frac{1}{R_{456789}} = \frac{1}{80} + \frac{1}{20}$
 $R_{456789} = 16\Omega$






⑥ $\frac{1}{R_{3456789}} = \frac{1}{R_3} + \frac{1}{R_{456789}}$
 $\frac{1}{R_{3456789}} = \frac{1}{48} + \frac{1}{16}$
 $R_{3456789} = 12\Omega$

⑦

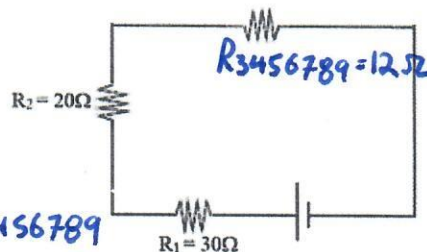$R_T = R_1 + R_2 + R_{3456789}$
 $R_T = 30 + 20 + 12$
 $R_T = 62\Omega$






#13)
Find V_s

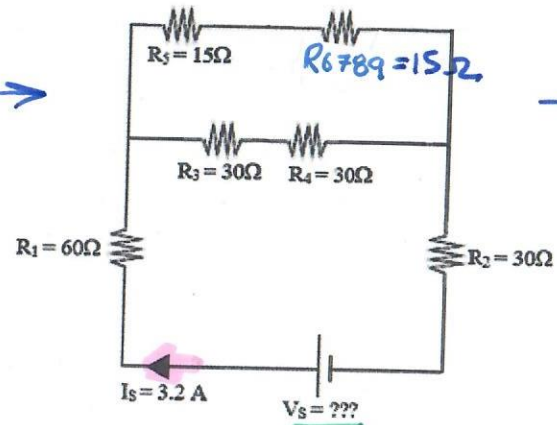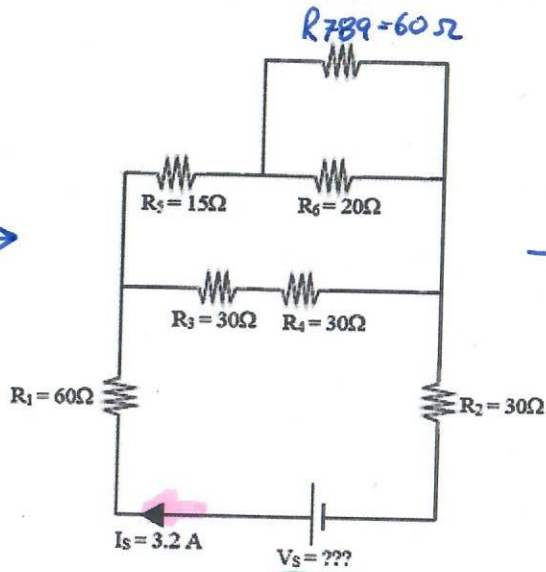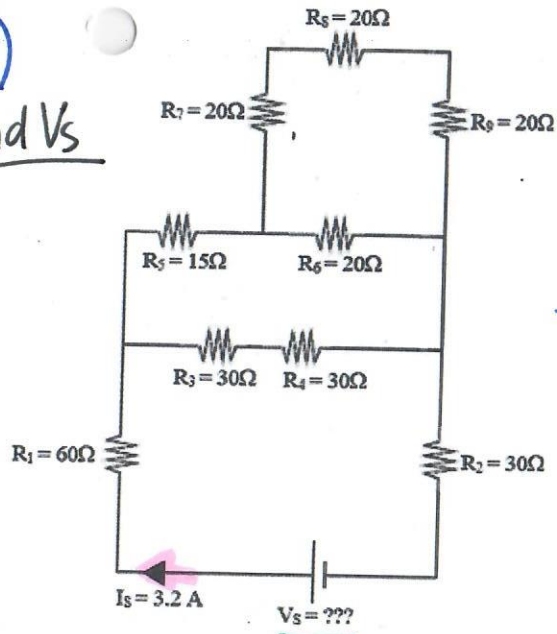

① $R_{789} = R_7 + R_8 + R_9$
 $R_{789} = 20 + 20 + 20$
 $R_{789} = 60\Omega$

② $\frac{1}{R_{6789}} = \frac{1}{R_6} + \frac{1}{R_{789}}$
 $\frac{1}{R_{6789}} = \frac{1}{20} + \frac{1}{60}$
 $R_{6789} = 15\Omega$

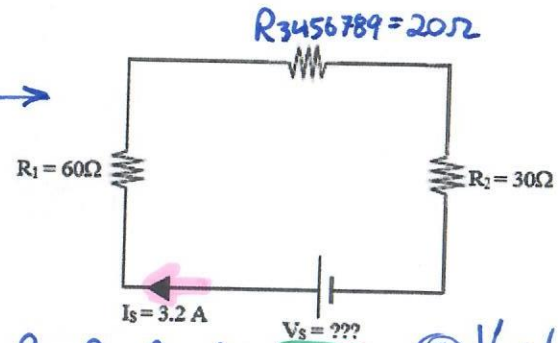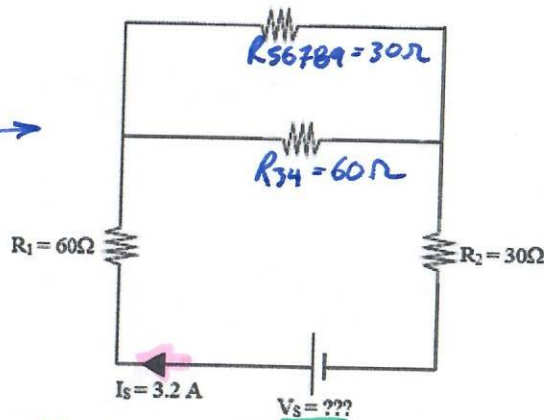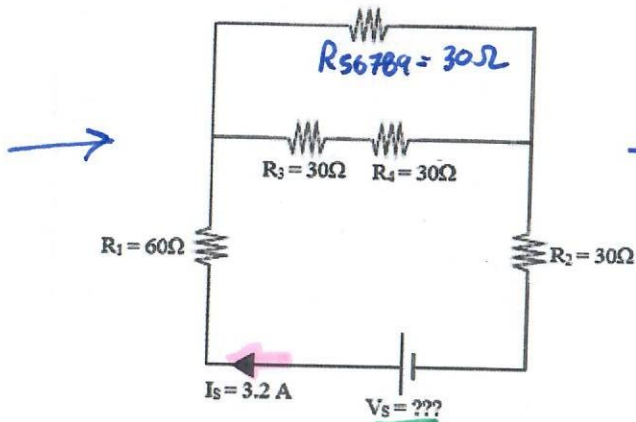③ $R_{56789} = R_5 + R_{6789}$
 $R_{56789} = 15 + 15$
 $R_{56789} = 30\Omega$



④ $R_{34} = R_3 + R_4$
 $R_{34} = 30 + 30$
 $R_{34} = 60\Omega$

⑤ $\frac{1}{R_{3456789}} = \frac{1}{R_{34}} + \frac{1}{R_{56789}}$
 $\frac{1}{R_{3456789}} = \frac{1}{60} + \frac{1}{30}$
 $R_{3456789} = 20\Omega$

⑥ $R_T = R_1 + R_2 + R_{3456789}$
 $R_T = 60 + 30 + 20$
 $R_T = 110\Omega$

⑦ $V_s = I_s R_T$
 $V_s = 3.2(110)$
 $V_s = 352V$